3.16 Fourier Transformation: Solving DEQs

Example 1: Low pass filter:



So according to the Kirchhoff equations we find for the current across the capacitor I_C

$$\frac{U_i(t) - U_o(t)}{R} = I_C(t) = C\dot{U}_o$$

After Fourier-Transformation this differential equation for U_o translates into

$$\frac{U_i(\omega) - U_o(\omega)}{R} = i\omega C U_o(\omega) \quad ,$$

i.e.

$$U_o(\omega) = \frac{U_i(\omega)}{1 + i\omega RC} := A(\omega)U_i(\omega) \quad ,$$

which is the response to a sinusoidally modulated input signal with frequency $\omega/2\pi$. Using the example IV for calculation of Fourier transformed we can find the original function A(t) of $A(\omega)$

$$A(t) = \mathcal{F}^{-1}\left\{\frac{1}{1+i\omega RC}\right\}$$
$$= \frac{\sqrt{2\pi}}{RC}\mathcal{F}^{-1}\left\{\frac{1}{\sqrt{2\pi}}\frac{1}{\frac{1}{RC}+i\omega}\right\} = \left\{\begin{array}{cc}\frac{\sqrt{2\pi}}{RC}e^{-\frac{t}{RC}} & \text{for } t \ge 0\\ 0 & \text{for } t < 0\end{array}\right.$$

According to the convolution theorem we find

$$U_o(t) = \mathcal{F}^{-1} \left\{ \frac{1}{1 + i\omega RC} U_e(\omega) \right\}$$
$$= \frac{1}{\sqrt{2\pi}} \int_{-\infty}^{+\infty} A(t - \tau) U_i(\tau) d\tau = \frac{1}{RC} \int_{-\infty}^{t} e^{-\frac{t - \tau}{RC}} U_i(\tau) d\tau$$

So this integral allows to calculate the response $U_o(t)$ of a low pass filter to an arbitrary input signal $U_i(t)$. Typically a filter is characterized in real space by the response to a step like perturbation

$$U_i(t) = \begin{cases} U_0 & \text{for } t \ge 0\\ 0 & \text{for } t < 0 \end{cases} , \qquad \qquad \uparrow \mathsf{U}_i(t), \ \mathsf{U}_o(t)$$

which for our case is

$$U_o(t) = \frac{1}{RC} \int_0^t e^{-\frac{t-\tau}{RC}} U_0 d\tau$$

= $U_0 \left(1 - e^{-\frac{t}{RC}}\right)$ 0 t

U.

In this example we calculated the two typical descriptions of a filter:

- the transfer function $A(\omega)$ in Fourier space
- the answer to a step like perturbation in real space, i.e. the transient.