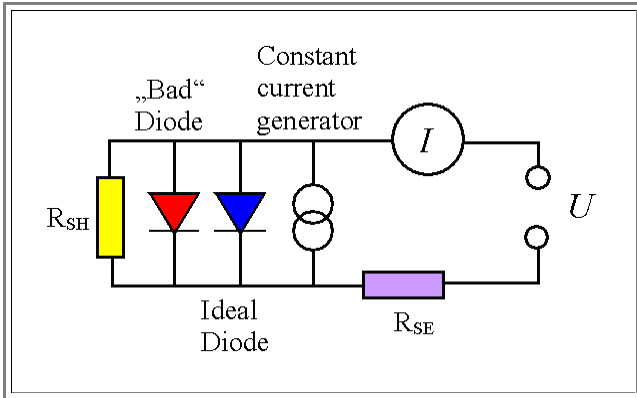


Exercise 8.1-3

IV Characteristics of Real Solar Cells


Let's consider a solar cell as described in the backbone, with a built in **series resistance** R_{SE} and a **shunt resistance** R_{SH}



- We have the equivalent circuit diagram as shown.
- The shunt resistance takes into account that the huge area of the **pn-junction** of a solar cell might have weak points (locally, e.g. at the edge) which short-circuits the junction somewhat. These defects are summarily described by a **shunt resistor**.
- The constant current source mimics the current generated in the junction by light. It simply defines a current value I_{ph} (not to be mixed up with the terminal current I) that is given by the light and added (with a negative sign) to the junction current, i.e. $I_{\text{junct}} = I_{\text{diode}}(U) - I_{ph}$. The photo current I_{ph} thus simply moves the total characteristics of the diode downwards on the current scale.

Take the following schematic curve of the **I-U**-characteristics as a reference and for the definition of the following terms:

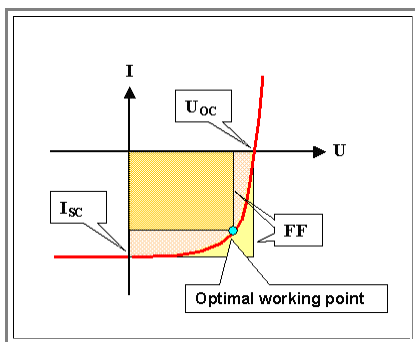- The **fill factor** is the relation between the area of the large yellow rectangle to the more orange area centered at the **optimal working point**.



Discuss qualitatively the influence of the **two resistors** (and, as a more minor point, the **ideality factor n**) on the **IV** characteristics with particular respect to:

- The **open-circuit voltage** U_{oc} .
- The **short-circuit current** I_{sc} .
- The **reverse dark current** if the solar cell is biased in the reverse direction.
- The **fill factor** FF (the degree of "rectangularism" of the characteristics).
- The **efficiency** η which is proportional to U_{oc} , I_{sc} , and FF , i.e.

$$\eta = \text{const} \cdot U_{oc} \cdot I_{sc} \cdot FF$$

[Link to the solution](#)